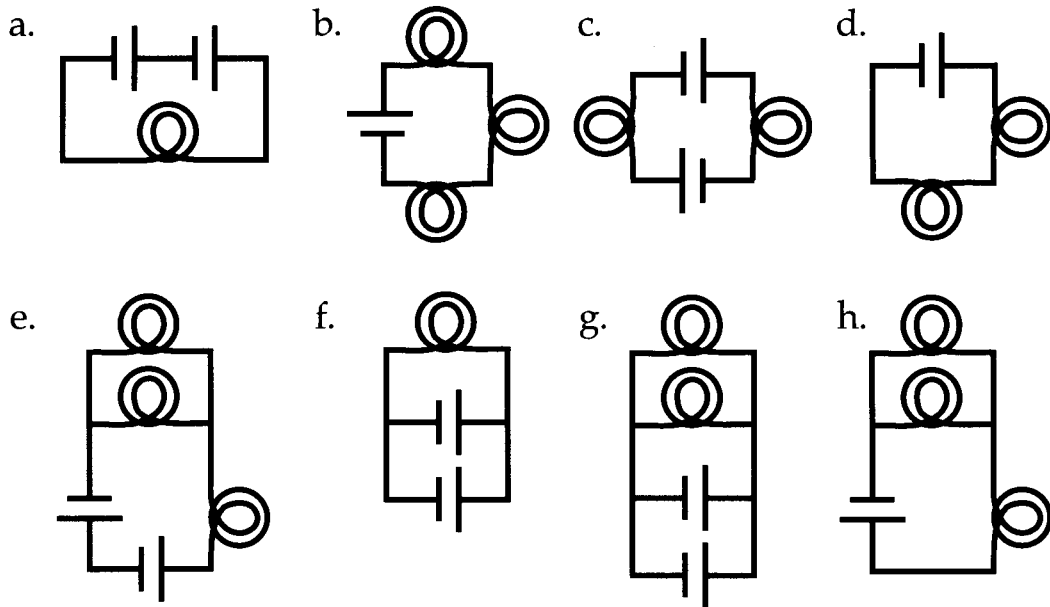


SERIES AND PARALLEL CIRCUITS B

4. Here are schematic diagrams for eight circuits. How would you describe each circuit?
 (See the description at the bottom of page 32 of the *Science Resources* book for an example.)



a. _____

b. _____

c. _____

d. _____

e. _____

f. _____

g. _____

h. _____